

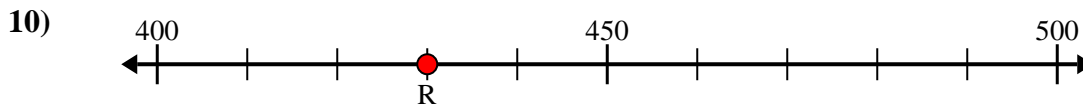
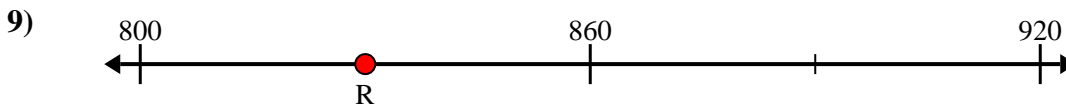
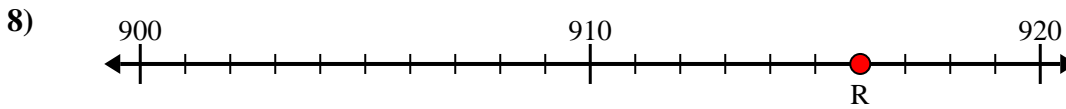
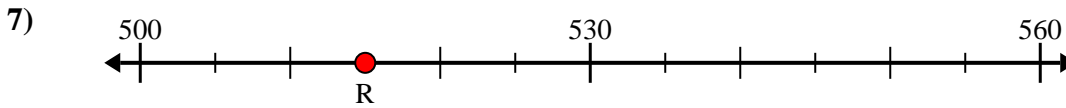
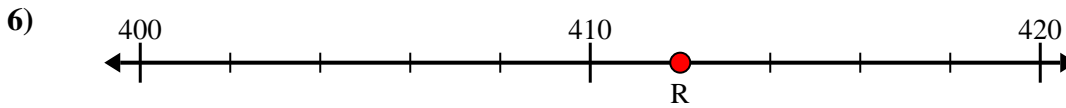
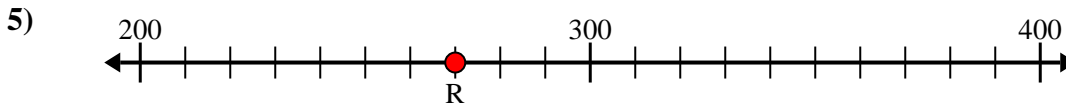
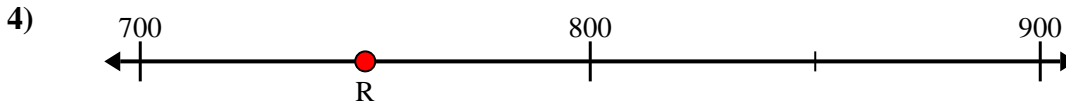
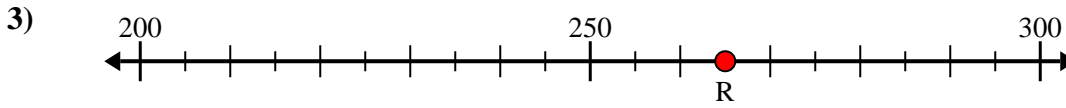


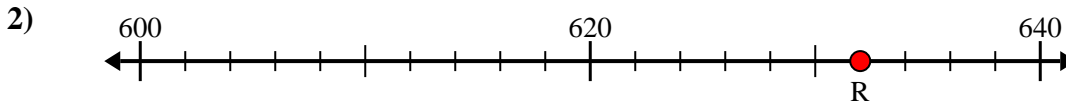

Encontrar el valor de R.











Respuestas

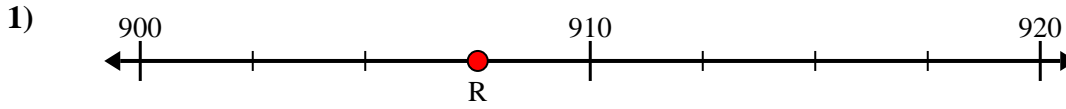

1. _____
2. _____
3. _____
4. _____
5. _____
6. _____
7. _____
8. _____
9. _____
10. _____



Encontrar el valor de R.

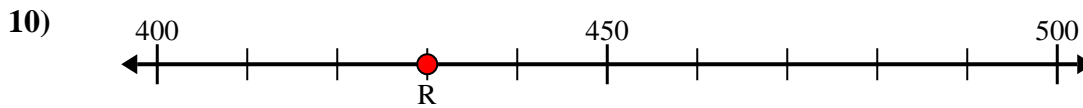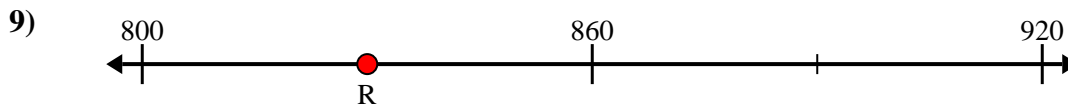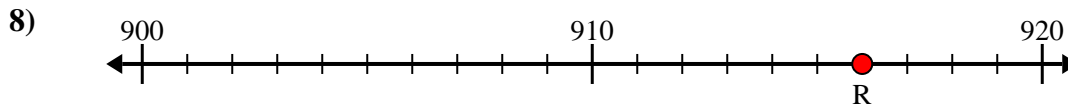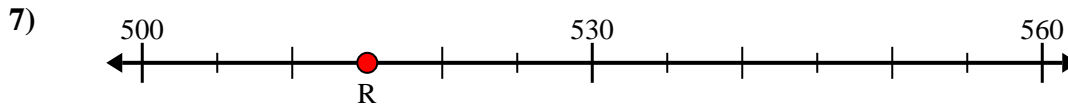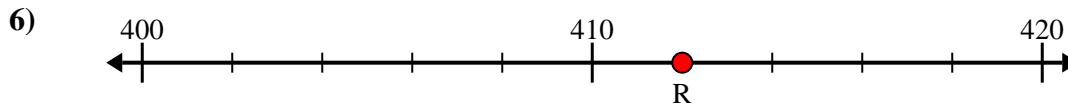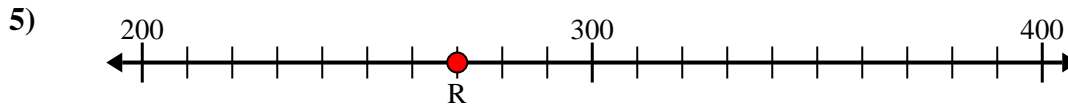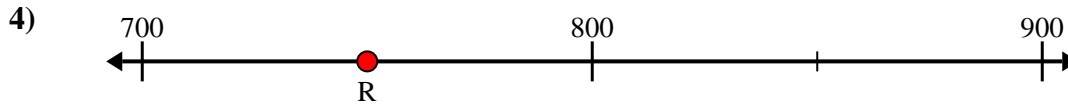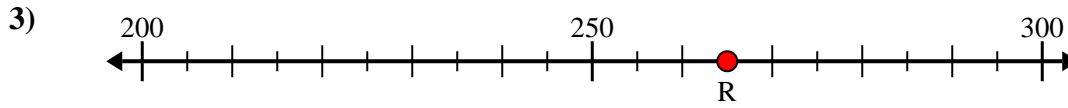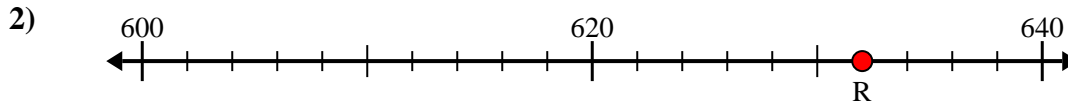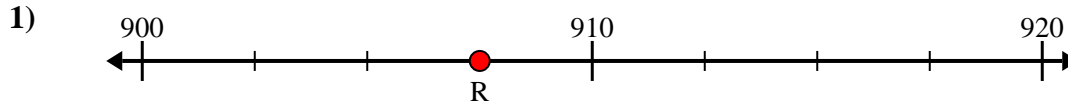

Respuestas

1. 907.5

2. 632

3. 265

4. 750

5. 270

6. 412

7. 515

8. 916

9. 830

10. 430