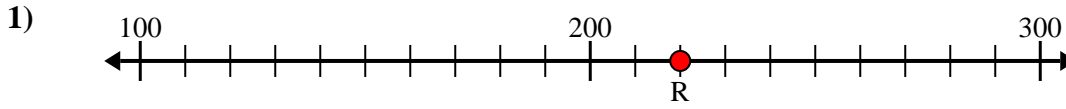





Encontrar el valor de R.


Respuestas




1. _____

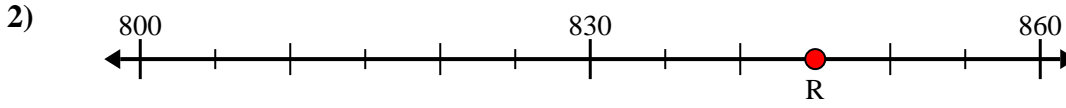


2. _____

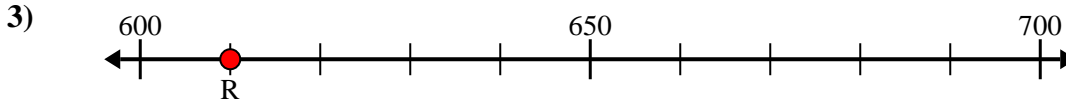


3. _____

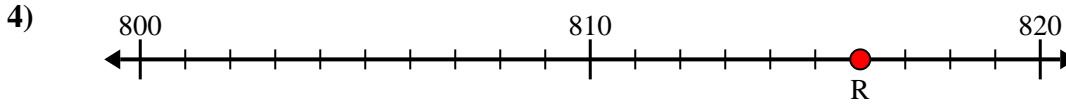


4. _____

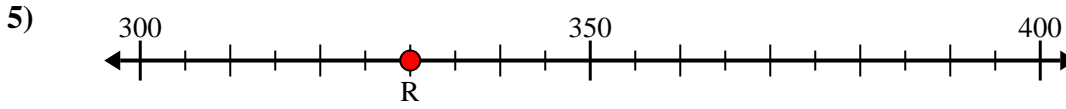


5. _____

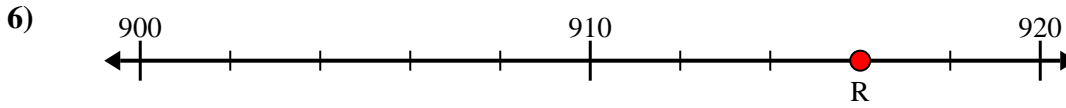


6. _____

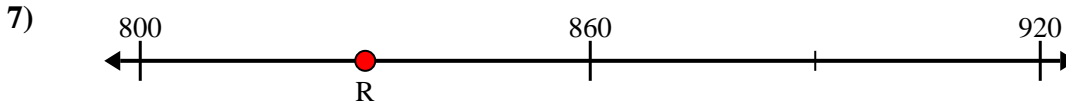


7. _____

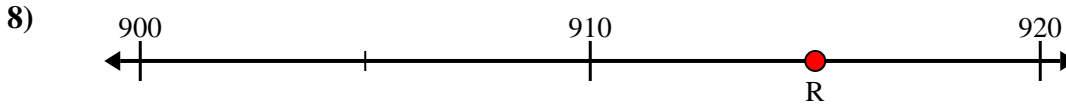

8. _____

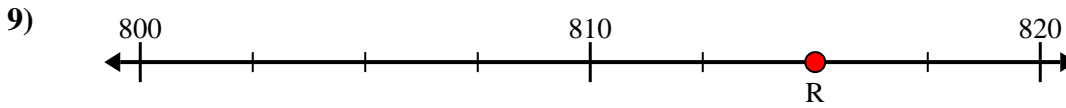











9. _____

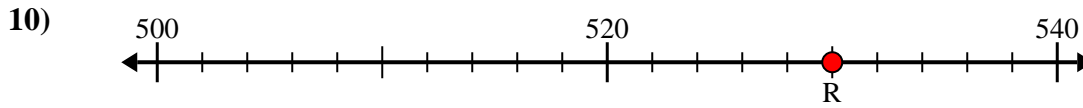

10. _____



Encontrar el valor de R.

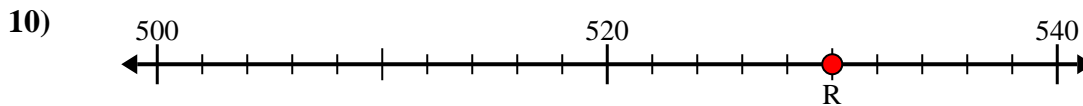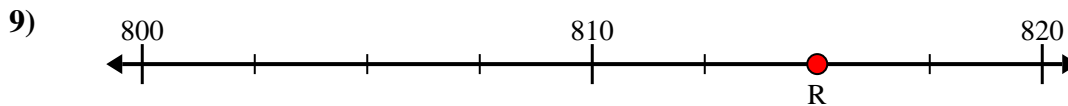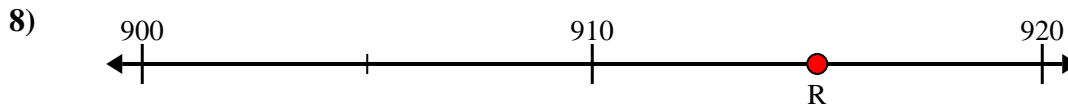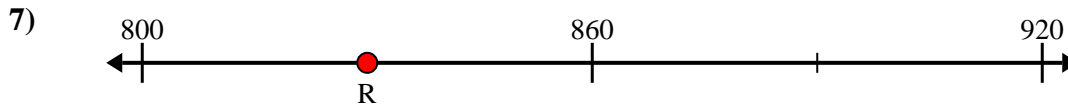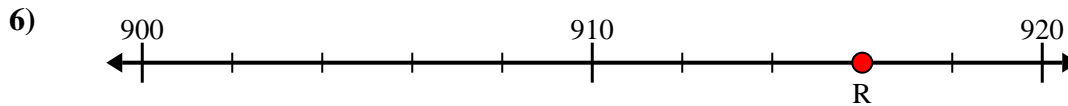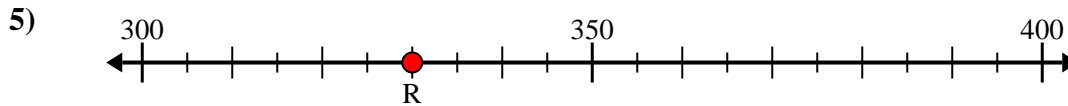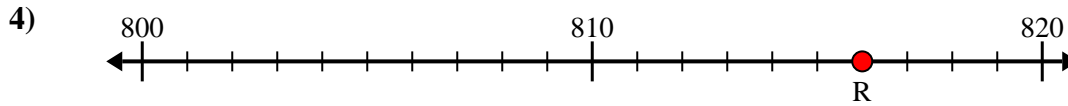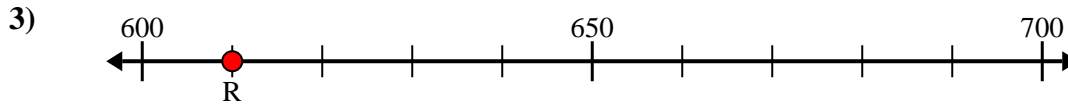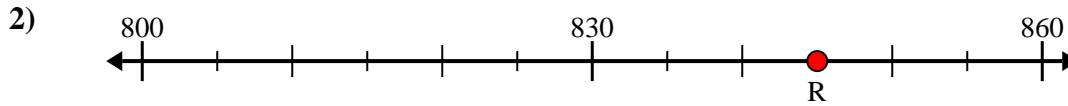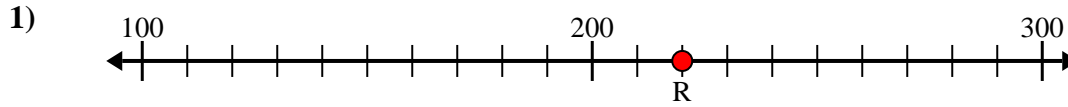

Respuestas

1. 220

2. 845

3. 610

4. 816

5. 330

6. 916

7. 830

8. 915

9. 815

10. 530